Akoizo Original Practice - 2027 Rotation Form 2

Division C | Circuit Lab | 50-minute written practice

Original Akoizo curriculum practice. This is not a historical tournament paper. Written build, CAD, lab and communication exercises supplement real practical preparation.

Name: _____ Date: _____

1. (2 points) Parallel resistors share…

Unit: Diagrams, nodes, series, parallel, and Ohm's law.
Worked-case data: Find Req for 100 Ω and 300 Ω in parallel on 6 V.

A. Voltage

B. Always current

C. Always power

D. Always resistance

Answer: _____

2. (2 points) A voltmeter connects…

Unit: Breadboards, multimeters, and a first virtual build.
Worked-case data: A known 100 Ω resistor has 2 V across it; an unknown in series has 4 V. Find the unknown.

A. As an intentional source short

B. Only instead of every wire

C. Only to ground alone

D. Across two nodes

Answer: _____

3. (2 points) NOT(A AND B) equals…

Unit: Digital logic and combinational circuits.
Worked-case data: For A=1, B=1, find half-adder sum and carry.

A. A OR B

B. (NOT A) AND B

C. A AND B

D. (NOT A) OR (NOT B)

Answer: _____

4. (2 points) An open switch can have…

Unit: Diagrams, nodes, series, parallel, and Ohm's law.
Worked-case data: Find Req for 100 Ω and 300 Ω in parallel on 6 V.

A. Infinite real power

B. Always zero voltage

C. Consumed charge

D. Voltage with zero current

Answer: _____

5. (2 points) Divider inference needs…

Unit: Breadboards, multimeters, and a first virtual build.
Worked-case data: A known 100 Ω resistor has 2 V across it; an unknown in series has 4 V. Find the unknown.

A. Zero source voltage

B. No known component

C. The same series current

D. Equal resistor values

Answer: _____

6. (4 points) Give half-adder equations.

Unit: Digital logic and combinational circuits.
Worked-case data: For A=1, B=1, find half-adder sum and carry.

Answer: _____
_____
_____

7. (4 points) Find 100 Ω parallel 100 Ω.

Unit: Diagrams, nodes, series, parallel, and Ohm's law.
Worked-case data: Find Req for 100 Ω and 300 Ω in parallel on 6 V.

Answer: _____
_____
_____

8. (4 points) What does meter loading mean?

Unit: Breadboards, multimeters, and a first virtual build.
Worked-case data: A known 100 Ω resistor has 2 V across it; an unknown in series has 4 V. Find the unknown.

Answer: _____
_____
_____

9. (4 points) Why is logical one not always 5 V?

Unit: Digital logic and combinational circuits.
Worked-case data: For A=1, B=1, find half-adder sum and carry.

Answer: _____
_____
_____

10. (4 points) Give a power check.

Unit: Diagrams, nodes, series, parallel, and Ohm's law.
Worked-case data: Find Req for 100 Ω and 300 Ω in parallel on 6 V.

Answer: _____
_____
_____

11. (2 points) A 8 V ideal battery drives a 4 ohm resistor. Find current.

Answer: _____
_____
_____

12. (2 points) A series pair has resistances 4 and 6 ohms. Find equivalent resistance.

Answer: _____
_____
_____

13. (2 points) Two identical 8 ohm resistors are placed in parallel. Find equivalent resistance.

Answer: _____
_____
_____

14. (2 points) An ideal resistor carries 2 A at 8 V. Find power.

Answer: _____
_____
_____

15. (2 points) A node has incoming currents 5 A and 2 A and one outgoing current. Find the outgoing current.

Answer: _____
_____
_____

16. (2 points) Explain why an ideal voltmeter is connected in parallel rather than used as a series current path.

Answer: _____
_____
_____

17. (2 points) Give the output of an AND gate for inputs 1 and 0, and explain.

Answer: _____
_____
_____

18. (2 points) A silicon diode is reverse biased below breakdown. Contrast its ideal current with a forward-biased conducting diode.

Answer: _____
_____
_____

19. (2 points) A closed DC loop has a 9 V source and a 4 V resistor drop. Find the remaining series resistor drop and state the governing law.

Answer: _____
_____
_____

20. (2 points) Two identical LEDs must be equally bright in a low-voltage teaching circuit. Explain why their branch currents and current-limiting arrangements matter.

Answer: _____
_____
_____