BullSO, University of South Florida - Repaired practice edition

Division B | Circuit Lab | Repair appendix

This appendix contains authored replacements and supplied written alternatives. It does not reconstruct unpublished historical material. For the listed item IDs, use this appendix instead of the archived wording and key.

Name: _____ Date: _____

repair-case. (4 points) Authored written substitute for unavailable source material: Why test all input combinations?

Unit: Digital logic and combinational circuits.
Worked-case data: For A=1, B=1, find half-adder sum and carry.

Answer: _____
_____
_____